 


# EECS151/251A

## Introduction to Digital Design and ICs

### Lecture 7: FSM & RISC-V Intro Sophia Shao



#### **Intel Launches \$1 Billion Fund to Build a Foundry Innovation Ecosystem**

SANTA CLARA, Calif.--(BUSINESS WIRE)-- What's New: Intel today announced a new \$1 billion fund to support early-stage startups and established companies building disruptive technologies for the foundry ecosystem. A collaboration between Intel Capital and Intel Foundry Services (IFS), the fund will prioritize investments in capabilities that accelerate foundry customers' time to market – spanning intellectual property (IP), software tools, innovative chip architectures and advanced packaging technologies. Intel also announced partnerships with several companies aligned with this fund and focused on key strategic industry inflections: enabling modular products with an open chiplet platform and supporting design approaches that leverage multiple instruction set architectures (ISAs), spanning x86, Arm and RISC-V.

<https://www.intc.com/news-events/press-releases/detail/1525/intel-launches-1-billion-fund-to-build-a-foundry>






- **Finite State Machine**
  - Introduction
  - **Moore vs Mealy FSM**
  - **FSM in Verilog**
- **RISC-V**
  - Introduction
  - **Datapath Elements**


# Moore vs Mealy FSMs

- Next state is always determined by current state and inputs
- Differ in output logic:
  - Moore FSM: outputs depend only on current state
  - Mealy FSM: outputs depend on current state and inputs

## Moore FSM

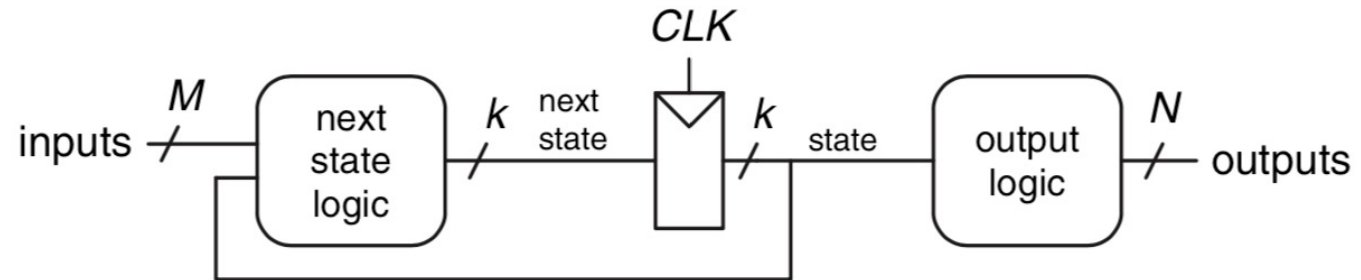


## Mealy FSM





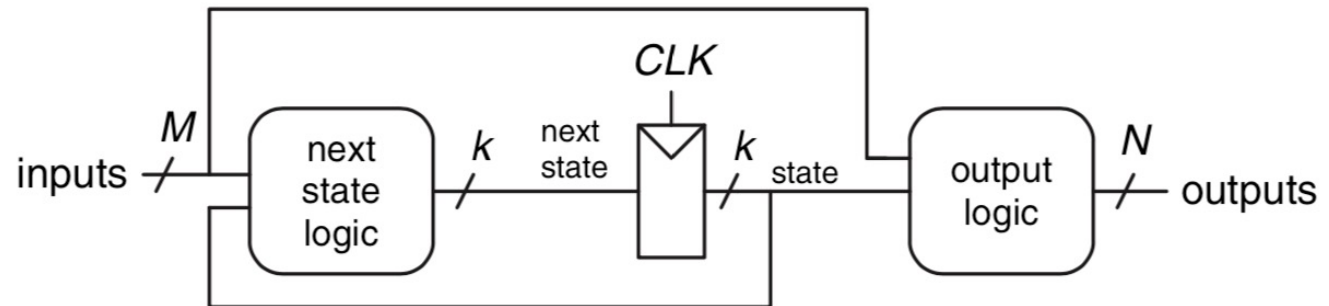

 
# Example: Edge Detector


- Input:
  - A bit stream that is received one bit at a time.
- Output:
  - 0/1
- Circuit:
  - Asserts its output to be true when the input bit stream changes from 0 to 1.





# Moore vs Mealy

 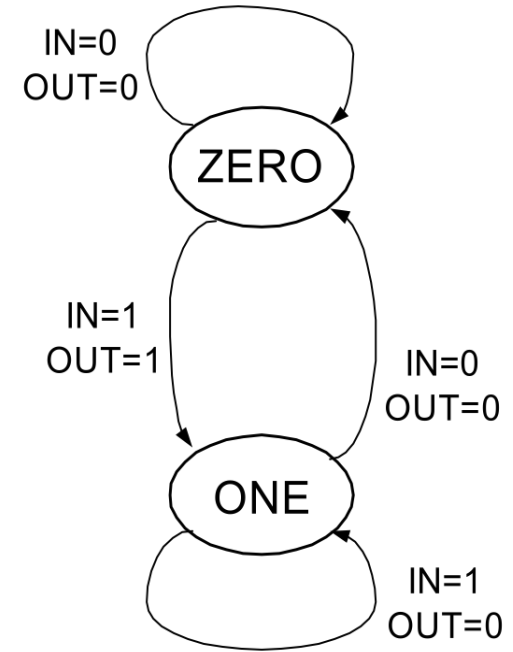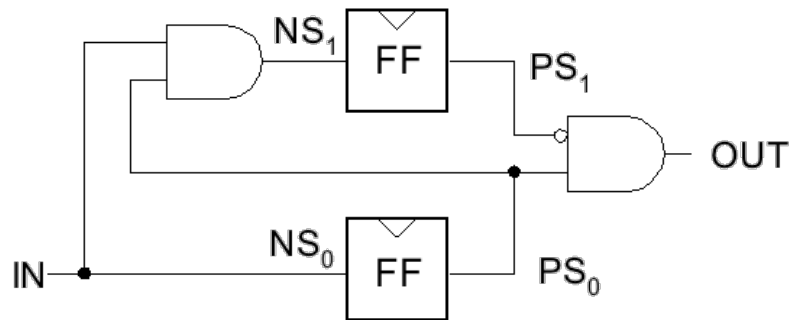  

# Edge Detection Timing Diagrams

 

  - Solution A (Moore) : both edges of output follow the clock
- Solution B (Mealy) : output rises with input rising edge and is asynchronous wrt the clock, output falls synchronous with next clock edge




# FSM Comparison

## *Solution A*
 
### **Moore Machine**


- output function only of current state
- maybe more states (why?)
- **synchronous** outputs
  - Input glitches not send at output
  - one cycle “delay”
  - full cycle of stable output



## *Solution B*

 
### **Mealy Machine**

- output function of both current = & input
- maybe fewer states
- **asynchronous** outputs
  - if input glitches, so does output
  - output immediately available
  - output may not be stable long enough to be useful (below):




If output of Mealy FSM goes through combinational logic before being registered, the CL might delay the signal and it could be missed by the clock edge (or violate set-up time requirement)
 
# Quiz: Which of the diagrams are **Moore** machines?




A.

 


B.

- A. AC
- B. BD
- C. AD
- D. BC

 

C.

 

D.





- **Finite State Machine**

- Introduction
- **Moore vs Mealy FSM**
- **FSM in Verilog**

- **RISC-V**


- Introduction
- **Datapath Elements**

# Implement FSM with Verilog


- Specify circuit function
  - Draw state transition diagram
  - Write down symbolic state transition table
  - Assign encodings (bit patterns) to symbolic states
- 
- Code as Verilog behavioral description
    - Use parameters to represent encoded states
    - Use separate always blocks for register assignment and combinational logic block
    - Use case statement for combinational logic.
      - Within each case section (state), assign outputs and next state based on inputs
      - Moore: outputs only dependent on states not on inputs

# Finite State Machine in Verilog

## State Transition Diagram

 

## Circuit Diagram

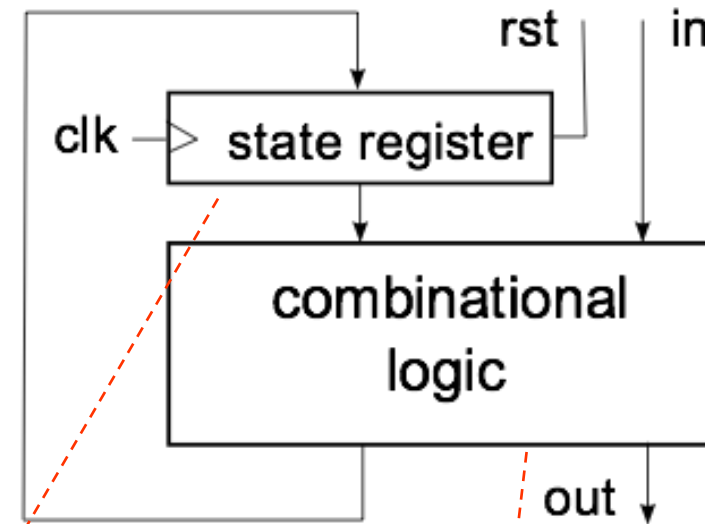

Holds a symbol to keep track of which bubble the FSM is in.

CL functions to determine output value and next state based on input and current state.

$out = f(in, \text{current state})$

$next\ state = f(in, \text{current state})$

# Finite State Machine in Verilog

```
module FSM1(clk, rst, in, out);  
  input clk, rst;  
  input in;  
  output out;
```

**Must use reset to force  
to initial state.**

```
// Defined state encoding:  
parameter IDLE = 2'b00;  
parameter S0 = 2'b01;  
parameter S1 = 2'b10;
```

**Constants local to  
this module.**

```
reg out;  
reg [1:0] current_state, next_state;
```


**out not a register, but assigned in always block**

**Combinational logic  
signals for transition.**

**The register to hold the "state" of the FSM.**

```
// always block for state register  
always @(posedge clk)  
  if (rst) current_state <= IDLE;  
  else current_state <= next_state;
```

 **A separate always block should be used for combination logic part of FSM. Next state and output generation. (Always blocks in a design work in parallel.)**




# Finite State Machine in Verilog (cont.)

```
// always block for combinational logic portion
always @(*)
case (current_state)
// For each state def output and next
  IDLE    : begin
              out = 1'b0;
              if (in == 1'b1) next_state = S0;
              else next_state = IDLE;
            end
  S0      : begin
              out = 1'b0;
              if (in == 1'b1) next_state = S1;
              else next_state = IDLE;
            end
  S1      : begin
              out = 1'b1;
              if (in == 1'b1) next_state = S1;
              else next_state = IDLE;
            end
  default: begin
              next_state = IDLE;
              out = 1'b0;
            end
endcase
endmodule
```

Each state becomes  
a case clause.

For each state define:  
Output value(s)  
State transition

 
Use "default" to cover unassigned state. Usually  
unconditionally transition to reset state.




Moore or  
Mealy?

# Edge Detector Example

## Moore Machine

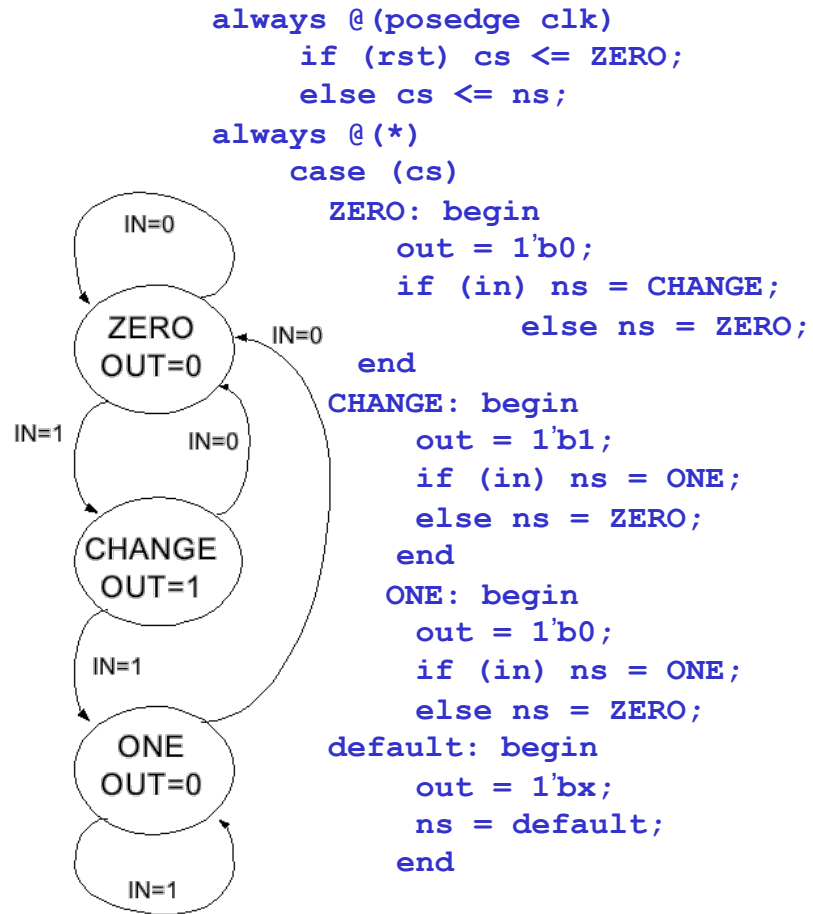

## Mealy Machine

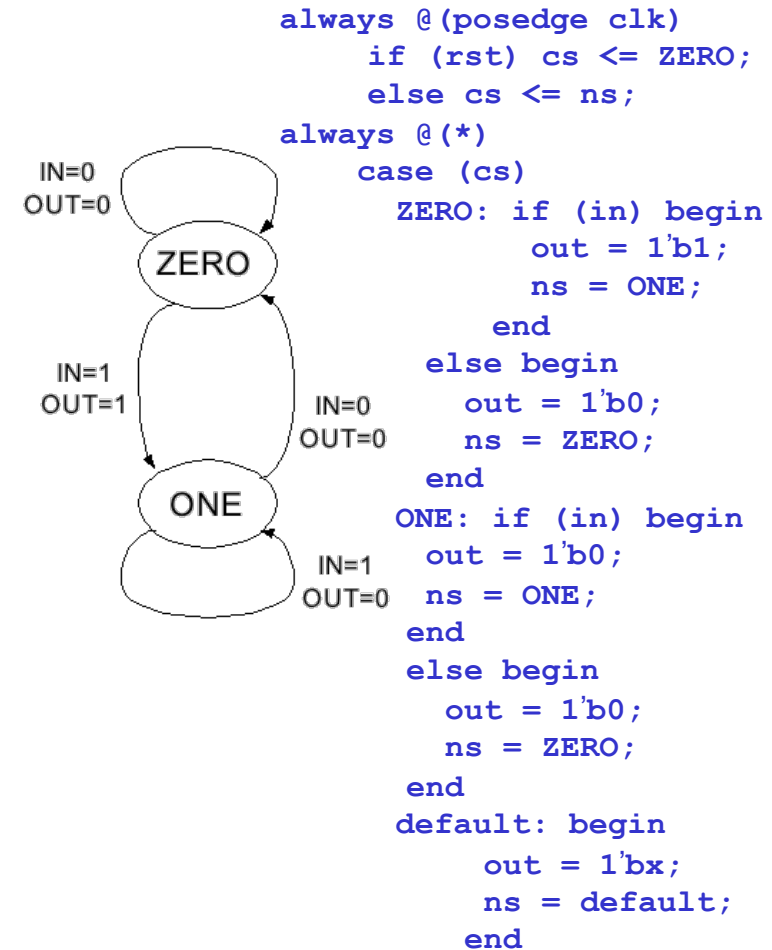

# Summary

- Sequential logic:
  - Memory: the outputs depend on both current and previous values of the inputs.
- Finite State Machine:
  - Registers to store current states
  - Combinational logic:
    - Compute the next state
    - Compute the outputs
- Moore vs Mealy FSM:
  - Moore: Outputs depend only on current state
  - Mealy: Outputs depend on current state and inputs

# Administrivia

- Mega-thread for each lab on Piazza.
  - Share your understanding (but not your design).
- Lab 4 starts this week.
  - Will be a 2-week lab.
- Homework 2 due this week.
- Homework 3 out.
- Midterm:
  - 3/1, Tuesday, in class.
  - Review session will be organized.





- **Finite State Machine**

- Introduction
- **Moore vs Mealy FSM**
- **FSM in Verilog**

- **RISC-V**

- Introduction
- **Datapath Elements**

# Berkeley RISC-V ISA


[www.riscv.org](http://www.riscv.org)

- An open, license-free ISA
  - Runs GCC, LLVM, Linux distributions, ...
  - RV32, RV64, and RV128 variants for 32b, 64b, and 128b address spaces
- Originally developed for teaching classes at Berkeley, now widely adopted
- Base ISA only ~40 integer instructions
- Extensions provide full general-purpose ISA, including IEEE-754/2008 floating-point
- Designed for extension, customization
- Developed at UC Berkeley, now maintained by RISC-V Foundation
- Open and commercial implementations
- RISC-V ISA, datapath, and control covered in CS61C; summarized here


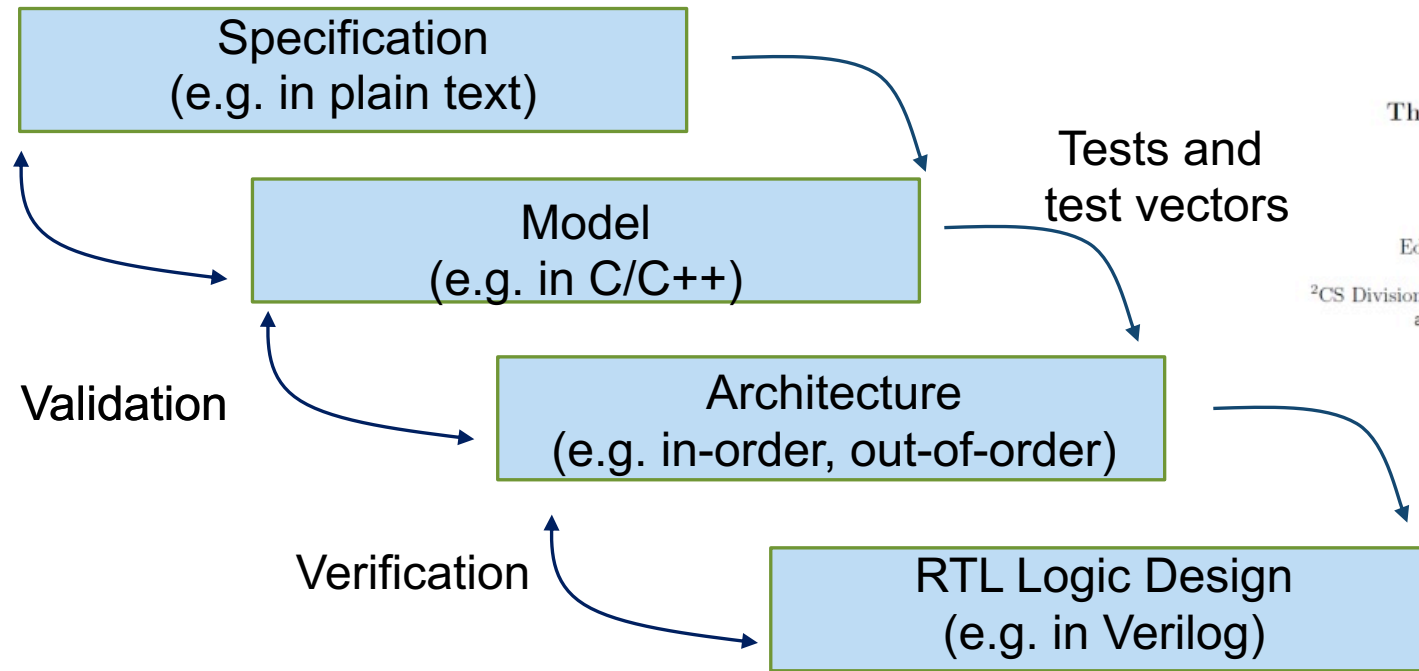
# RISC-V Processor Design

- Spec: Unprivileged ISA, RV32I (and a look at RV64I)




The RISC-V Instruction Set Manual  
Volume I: Unprivileged ISA  
Document Version 20190608-Base-Ratified

Editors: Andrew Waterman<sup>1</sup>, Krste Asanović<sup>1,2</sup>  
<sup>1</sup>SiFive Inc.,

<sup>2</sup>CS Division, EECS Department, University of California, Berkeley  
andrew@sifive.com, krste@berkeley.edu  
June 8, 2019

- Tests provided as a part of the project
- Architecture: Single-cycle and pipelined in-order processor
  - Expanded from CS61C
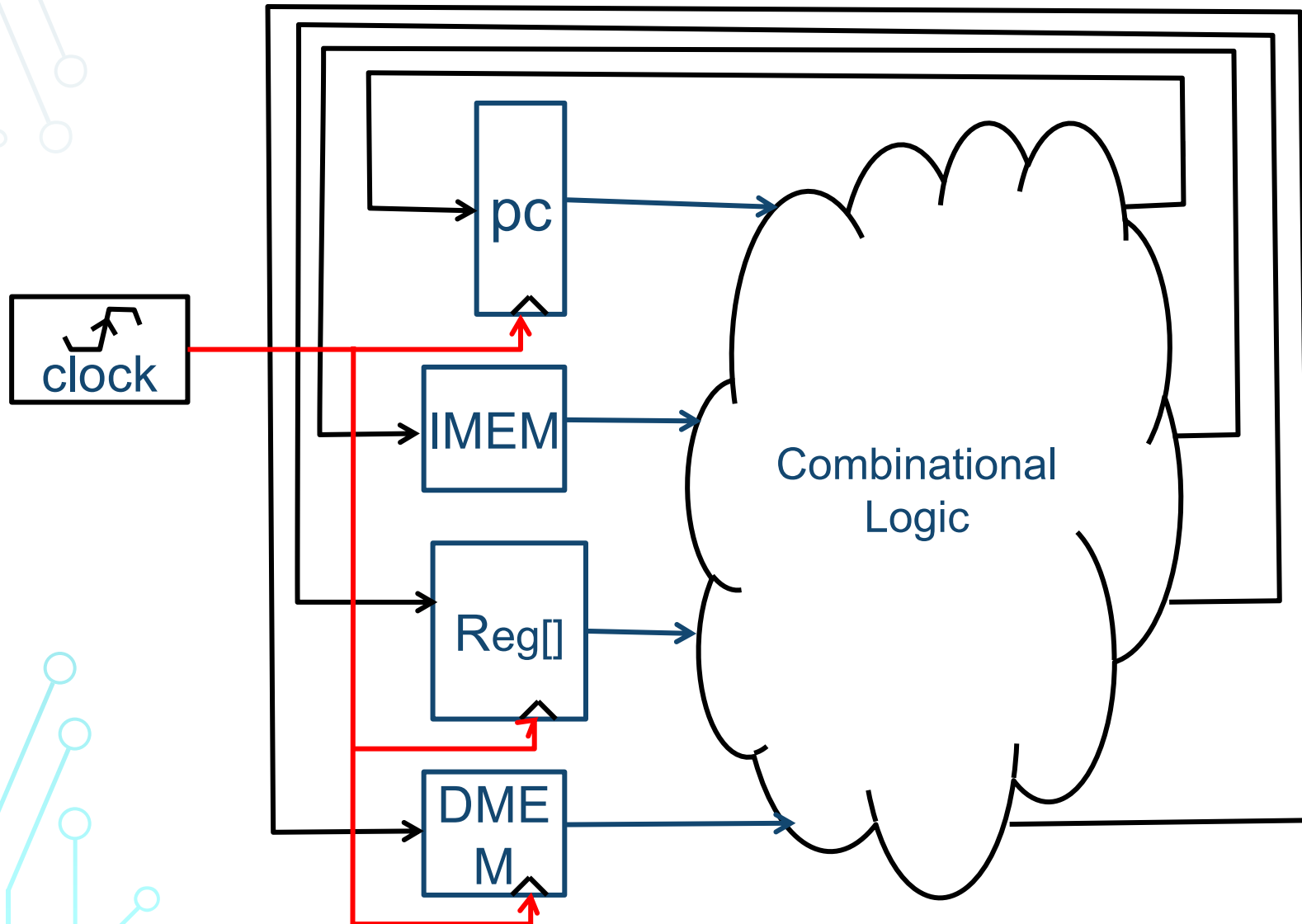
# One-Instruction-Per-Cycle RISC-V Machine



- On every tick of the clock, the computer executes one instruction
- Current state outputs drive the inputs to the combinational logic, whose outputs settles at the values of the state before the next clock edge
- At the rising clock edge, all the state elements are updated with the combinational logic outputs, and execution moves to the next clock cycle

# State Required by RV32I ISA

Each instruction reads and updates this state during execution:

- Registers (**x0** . . **x31**)
  - Register file (*regfile*) **Reg** holds 32 registers x 32 bits/register: **Reg**[0] . . **Reg**[31]
  - First register read specified by *rs1* field in instruction
  - Second register read specified by *rs2* field in instruction
  - Write register (destination) specified by *rd* field in instruction
  - **x0** is always 0 (writes to **Reg**[0] are ignored)
- Program counter (**PC**)
  - Holds address of current instruction
- Memory (**MEM**)
  - Holds both instructions & data, in one 32-bit byte-addressed memory space
  - We'll use separate memories for instructions (**IMEM**) and data (**DMEM**)
    - *These are placeholders for instruction and data caches*
  - Instructions are read (*fetched*) from instruction memory
  - Load/store instructions access data memory

# Stages of the Datapath : Overview

- **Problem:**

- A single, “monolithic” CL block that “executes an instruction” (performs all necessary operations beginning with fetching the instruction and completing with the register access) is be too bulky and inefficient


- **Solution:**

- Break up the process of “executing an instruction” into stages, and then connect the stages to create the whole datapath
  - smaller stages are easier to design
  - easy to optimize (change) one stage without touching the others (modularity)

# Five Stages of the Datapath

- Stage 1: *Instruction Fetch (IF)*
- Stage 2: *Instruction Decode (ID)*
- Stage 3: *Execute (EX) - ALU* (Arithmetic-Logic Unit)
- Stage 4: *Memory Access (MEM)*
- Stage 5: *Write Back to Register (WB)*


# Basic Phases of Instruction Execution

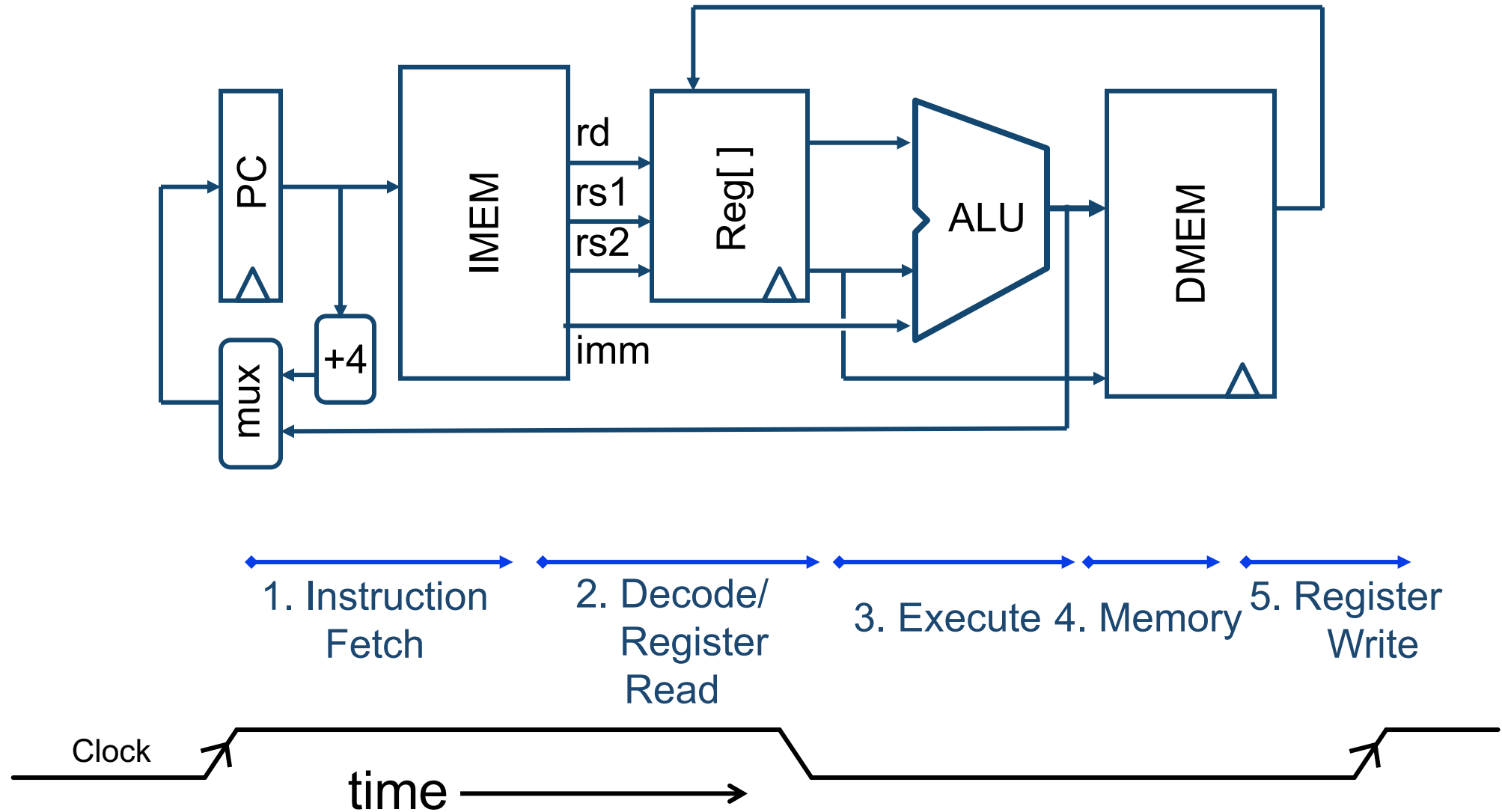




# Datapath Components: Combinational


- Combinational Elements

 

**Adder**

 


**Multiplexer**

 

**ALU**

# Datapath Elements: State and Sequencing (1/4)

- Register

 


```
always @(posedge clk)
    if (wen) dataout <= datain;
endmodule
```

- Write Enable:
  - Negated (or deasserted) (0):  
Data Out will not change
  - Asserted (1): Data Out will become  
Data In on positive edge of clock
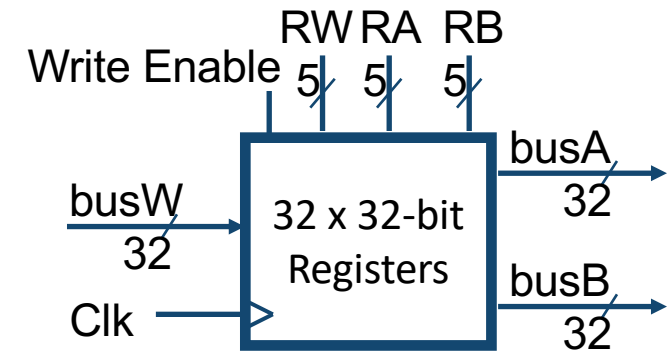
# Datapath Elements: State and Sequencing (2/4)

- Register file (regfile, RF) consists of 32 registers:
  - Two 32-bit output busses: busA and busB
  - One 32-bit input bus: busW
  - x0 is wired to 0
- Register is selected by:
  - RA (number) selects the register to put on busA (data)
  - RB (number) selects the register to put on busB (data)
  - RW (number) selects the register to be written via busW (data) when Write Enable is 1
- Clock input (clk)
  - Clk input is a factor ONLY during write operation
  - During read operation, behaves as a combinational logic block:
    - RA or RB valid  $\Rightarrow$  busA or busB valid after “access time.”





# Datapath Elements: State and Sequencing (3/4)

- Reg file in Verilog

```

 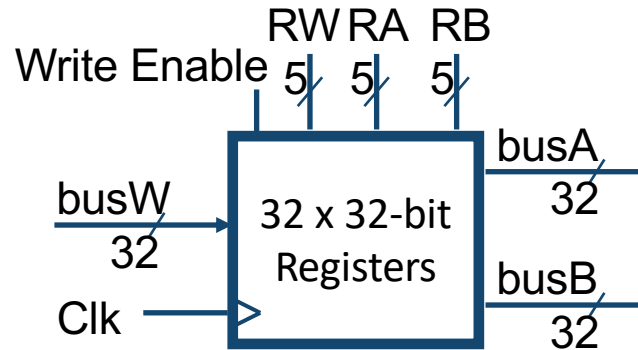
module rv32i_regs (
    input clk, wen,
    input [4:0] rw,
    input [4:0] ra,
    input [4:0] rb,
    input [31:0] busw,
    output [31:0] busa,
    output [31:0] busb
);
    reg [31:0] regs [0:31];
    always @(posedge clk)
        if (wen) regs[rw] <= busw;
    assign busa = (ra == 5'd0) ? 32'd0: regs[ra];
    assign busb = (rb == 5'd0) ? 32'd0: regs[rb];
endmodule
    
```



- How does RV64I register file look like?
 
# Datapath Elements: State and Sequencing (4/4)

- “Magic” memory
  - One input bus: Data In
  - One output bus: Data Out
- Memory word is found by:
  - For Read: Address selects the word to put on Data Out
  - For Write: Set Write Enable = 1: address selects the memory word to be written via the Data In bus
- Clock input (CLK)
  - CLK input is a factor ONLY during write operation
  - During read operation, behaves as a combinational logic block: Address valid  $\Rightarrow$  Data Out valid after “access time”
- Real memory later in the class





- **Finite State Machine**
  - Introduction
  - **Moore vs Mealy FSM**
  - **FSM in Verilog**
- **RISC-V**
  - Introduction
  - **Datapath Elements**

# Summary

- State machines:
  - Specify circuit function
  - Draw state transition diagram
  - Write down symbolic state-transition table
  - Assign encodings (bit patterns) to symbolic states
  - Code as Verilog behavioral description
- RISC-V processor
  - A large state machine
  - Datapath + control